

Lecture 10: Registers and counters

Chapter 6.1, 6.6

Objectives

- Analysis of *registers* and *counters* as an integration of sequential circuits
 - Sequential functional blocks

Sequential functional blocks

- Sequential circuits that perform certain specific functions
- Structured circuits, with multiple stages or cells that are (close to) identical
- Expansion of circuits is simple
- Registers and counters
 - Registers: store information during data processing
 - Counters: assist in sequencing data processing

Outline

- Registers
- Counters

Registers (1)

- Composed of flip-flops
 - n-bit register: n flip-flops, with one flip-flop storing 1 bit binary information
- Combined with combinational logic gates
 - Flip-flops hold data
 - Combinational logic gates determine the new or transformed data to be transferred into flip-flops
- Useful to store and manipulate data information


Registers (2)

Example: a 4-bit register

4 D flip flops, with clock signal and clear input

Clear input:
Clear = 1 to clear flip-flops' values to 0;
Clear = 0 during normal operations

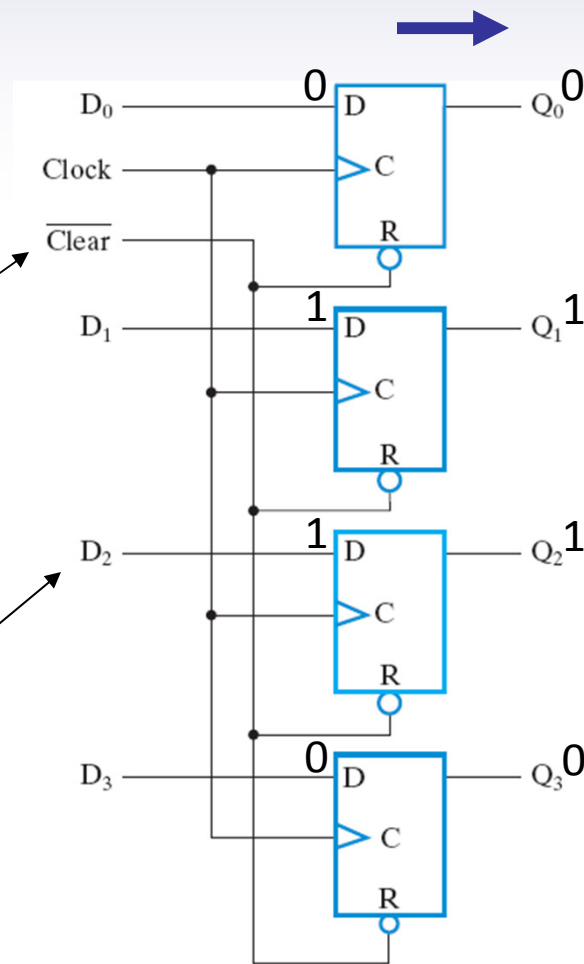
D inputs:
Data (binary values) to be stored



 (a) Logic diagram

Positive clock edge:
Transfer 4-bit binary information into the register (a.k.a. loading a register)



Parallel loading: all bits of registers are loaded with a common clock pulse



Graphical symbol

Registers with load control

  - We want to keep the contents of register unchanged
- Method: prevent clock signal entering the circuit
- Load control input: a load control (Load) combined with the clock signal
- Also known as “clock gating”




Clock skewing effect


- Clock gating may produce *clock skew*
 - Clock skewing effect: clock signals arrive at different flip-flops or registers at different time
- Flip-flops with *clock gating* receive clock signal later than others without clock gating
 - Gate delays exist on logic gates, and hence on the clock signals
- Not desirable
 - Should ensure all flip-flops are triggered at the same time in a truly synchronous system

D flip-flop with enable

 
- Use 4 *D flip-flops with enable* to build a 4-bit register
- During a positive clock edge
 - Load = 1: data in D_0 to D_3 are transferred into the register
 - Load = 0: current value remains in the register
- Avoids clock skewing effect
 - Clock pulses are applied continuously to input C of flip-flops



(a)

 



(b)

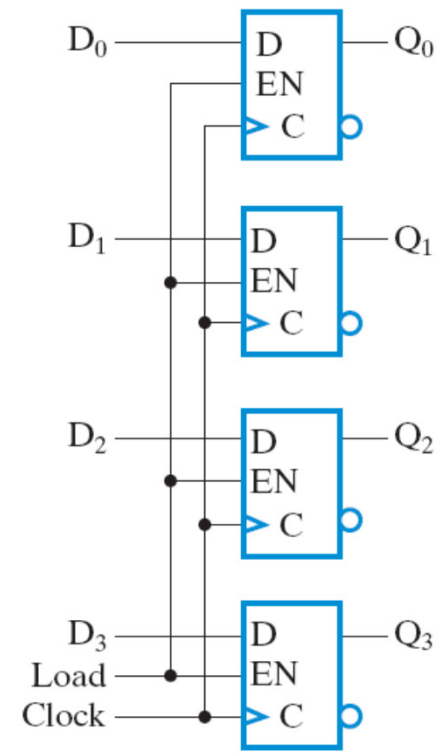


(c)

Shift registers

  - Operations: shift the stored bits laterally in one or both directions
- Implementation
 - Chain of flip-flops, output of one flip-flop connects to input of the next flip-flop
 - Common clock pulse to all flip-flops



Shift register with parallel load (1)

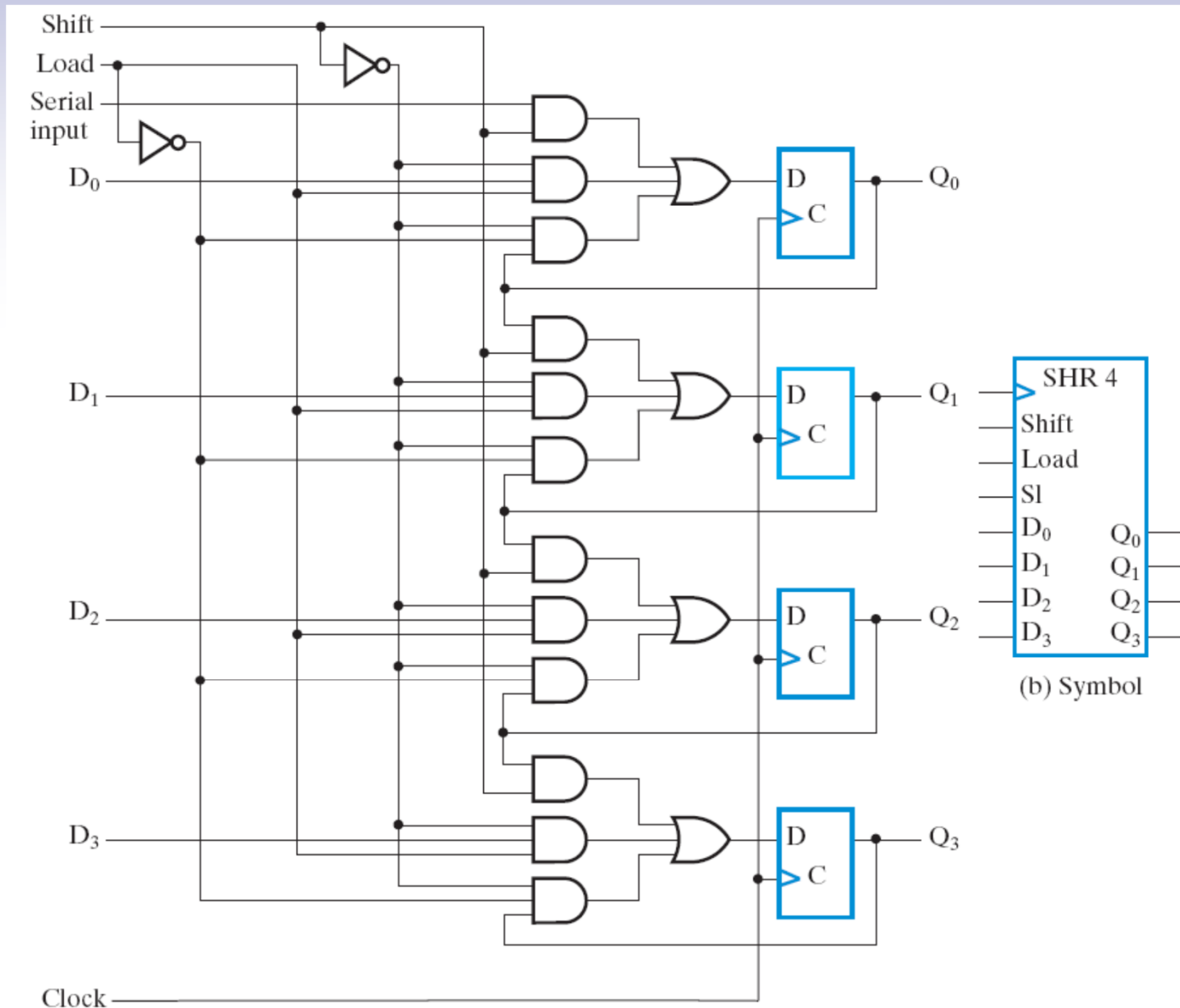

Shift register with parallel load (2)

- Shift = 1 → enable first AND gate
 - Bit shifts down from Q_0 to Q_3 (Q_0 = serial input)
- Shift = 0 & Load = 1 → enable second AND gate
 - Load parallel data D_0 to D_3 into registers (Q_0 to Q_3)
- Shift = 0 & Load = 0 → enable third AND gate
 - Q_i connected back to flip-flop i (no change)

Shift	Load	Operation
0	0	No change
0	1	Load parallel data
1	X	Shift down from Q_0 to Q_3

Bidirectional shift register (2)

- Shifting data in both directions
- A multiplexer at each stage i
 - Selection inputs: control operation of the register at stage i

Mode control		Register Operation
S_1	S_0	
0	0	No change
0	1	Shift down
1	0	Shift up
1	1	Parallel load

Outline


- Registers
- Counters

Counters

- A register that goes through a predetermined sequence of binary states upon application of clock pulse
 - States are the “counting values”
 - Combinational logic gates are connected in a way to produce the state sequence
- Binary counter
 - Follows binary number sequence
 - n -bit binary counter: n flip-flops, counts from 0 to $2^n - 1$
- Function
 - To sequence and control operations in a digital system
- Two categories
 - Synchronous vs. asynchronous (ripple counters)

4-bit binary ripple counter (1)

 - Example: built by positive edge-triggered D flip-flops
- Behaviour
 - Output of a flip-flop is complemented upon a positive edge to C input
 - D flip-flops are triggered at different times
- Implementation
 - **D input:** complemented output of itself
 - **C input of first flip-flop:** clock pulse
 - **C input of other flip-flops:** complemented output of the previous (less significant) flip-flop



4-bit binary ripple counter (2)

D input value?

$Q_i: 1 \rightarrow 0$, Q_{i+1} is complemented
Hence, D input is complement of own output

How about the implementation of a downward counter?

C input value?

Flip-flop in bit position $i+1$ should be triggered at a time when Q_i changes from 1 to 0

Flip-flops are positive edge triggered (i.e., triggered when C changes from 0 to 1)

Hence, C input of flip-flop $i+1$ = complemented Q_i

Upward Counting Sequence				Downward Counting Sequence			
Q_3	Q_2	Q_1	Q_0	Q_3	Q_2	Q_1	Q_0
0	0	0	0	1	1	1	1
0	0	0	1	1	1	1	0
0	0	1	0	1	1	0	1
0	0	1	1	1	1	0	0
0	1	0	0	1	0	1	1
0	1	0	1	1	0	1	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	0	0
1	0	0	0	0	1	1	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	0	1
1	0	1	1	0	1	0	0
1	1	0	0	0	0	1	1
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	0	0

4-bit binary ripple counter (3)

- Advantages
 - Simple hardware
- Disadvantages
 - Asynchronous, hence is delay dependent and unreliable
 - Clock applies to C input of one flip-flop only
 - Slow in counting one state: changes in each bit can occur only after the less significant bit has changed
- Synchronous binary counter
 - One common clock pulse triggers all flip-flops at the same time
 - Serial and parallel counters


Synchronous serial counter

- Upon a positive clock edge
 - Q_i is complemented only when $Q_{i-1}, Q_{i-2}, \dots, Q_1, Q_0$ are all 1s
 - Otherwise, Q_i is unchanged
- Implementation: XOR gate
 - Take complement if less significant Q s are 1

$$Q_i(t + 1) = D_i(t)$$

$$= Q_i(t) \oplus (Q_{i-1}(t) \cdot Q_{i-2}(t) \cdot \dots \cdot Q_1(t) \cdot Q_0(t) \cdot EN)$$


AND operation is performed serially

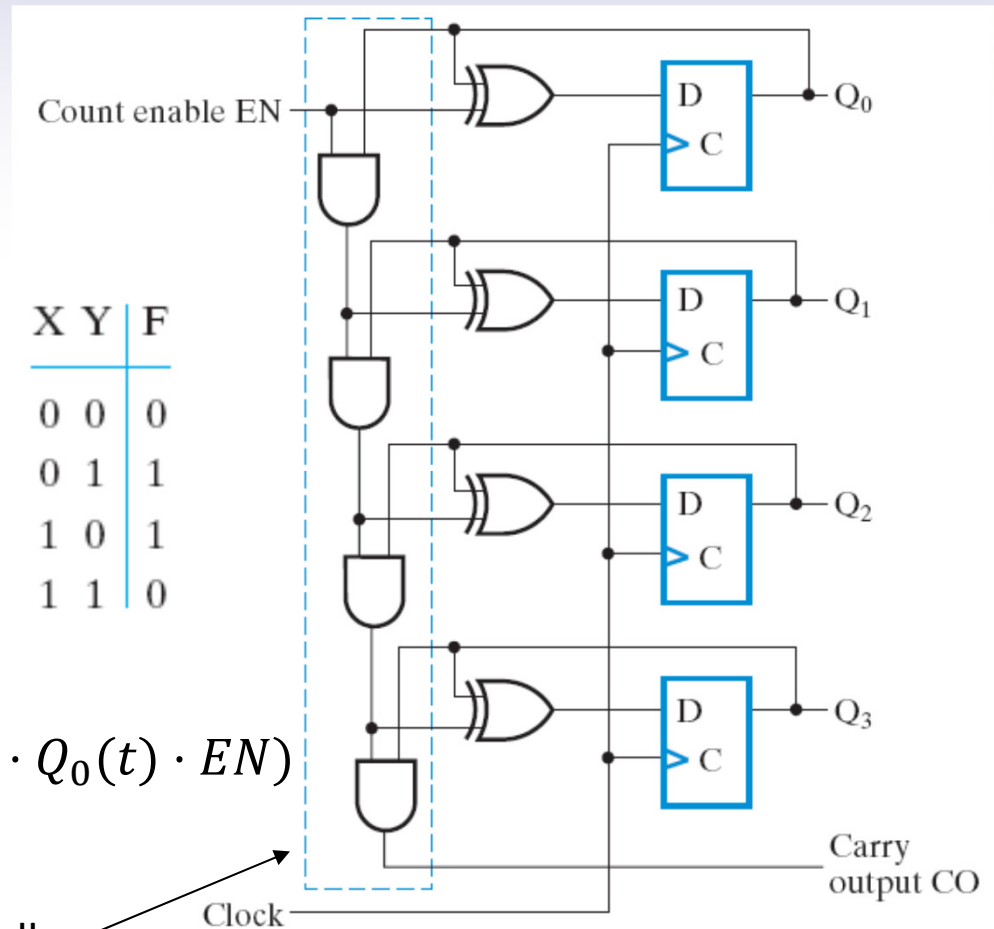


Synchronous parallel counter

Another implementation for the logic:
 
$$Q_{i-1}(t) \cdot Q_{i-2}(t) \cdot \dots \cdot Q_1(t) \cdot Q_0(t) \cdot EN$$



 Logic diagram of 4-bit synchronous binary counter



Binary counter with parallel load

Allows an initial value (binary number), e.g., $D_3:D_0$ to be loaded prior to counting

Selection input logic

Gates for counting


Gates for selection logic

Selection based on (1) Load, (2) Count:

Load = 1: $D_3:D_0$ loaded into counter

Load = 0 & Count = 1: count

Load = 0 & Count = 0: hold

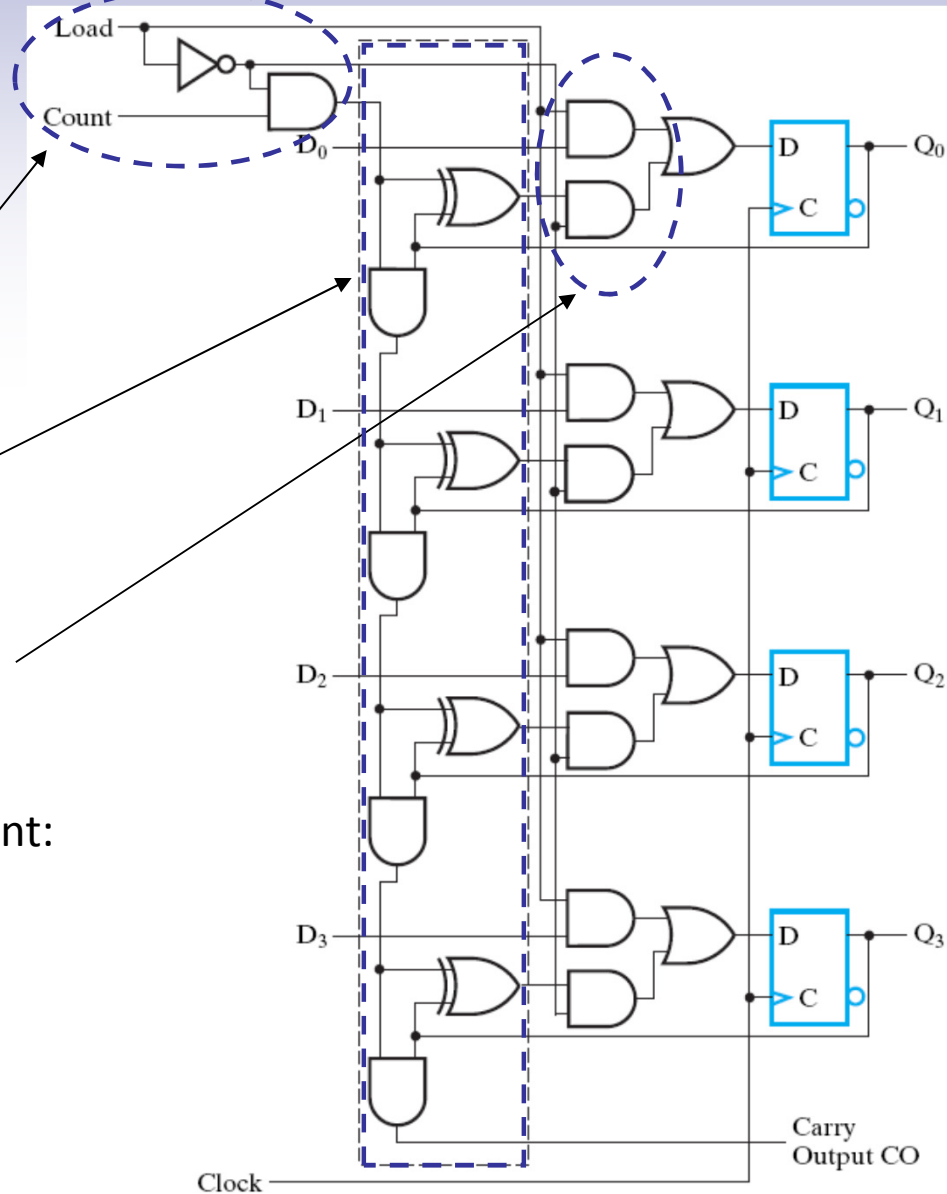


Divide-by-N counter

- Counters that go through a repeated sequence of N states
- Examples
 - BCD counters
 - Counters with arbitrary sequence of states

BCD counter

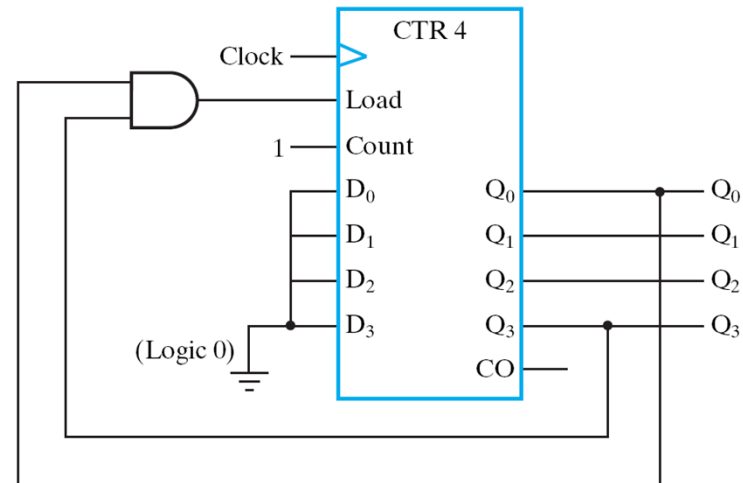- Implementation
 - Use a binary counter with parallel load
 - Set Load = 1 when Q = 1001
 - Hence, count again from 0000 when 1001 is reached



Counter with arbitrary count (1)

- Study Guide Worked Example 10.2

Counter with arbitrary count (2)

- Example: counter that counts the sequence: 000, 001, 010, 100, 101, 110, and reset to 000

Present State			Next State		
A	B	C	DA = A(t+1)	DB = B(t+1)	DC = C(t+1)
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	0	0	0

Flip-flop input equations:


$$D_A = A \oplus B$$

$$D_B = C$$

$$D_C = \overline{B} \overline{C}$$

Counter with arbitrary count (2)

 Logic diagram of a counter with arbitrary count



Summary and acknowledgment

- Registers are set of interconnected flip-flops with combinational logic
- Counters go through a predetermined sequence of binary states
- Implementation of different registers and counters are studied
- Reference
 - Logic and Computer Design Fundamentals (5/e)