

Lecture 3: Combinational Logic Design

Chapter 3.1 – 3.2

Objectives

- Discuss the procedures in designing a combinational circuit based on the problem specification
- Discuss the techniques in *technology mapping* of a circuit to NAND and NOR gate technologies
- Verify a logic circuit implementation through logic analysis process

Outline


- Combinational circuit design procedures
- BCD-to-excess-3 code converter
- BCD-to-seven-segment decoder
- Hierarchical design
- Technology mapping and verification

Outline

- **Combinational circuit design procedures**
- BCD-to-excess-3 code converter
- BCD-to-seven-segment decoder
- Hierarchical design
- Technology mapping and verification

Design procedures (1)

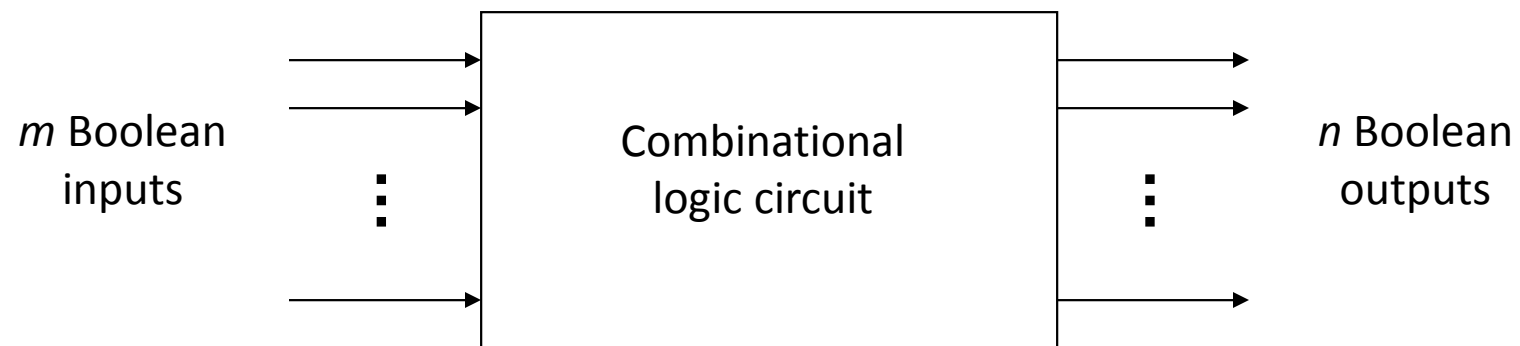- Five procedures to design a combinational circuit
 - Combinational circuit: a circuit made up of logic gates, which produces an output given some inputs
 - Specification → Formulation → Optimization → Technology mapping → Verification
- Objective
 - Given the problem specification, draw the logic circuit diagram of the combinational circuit



Design procedures (2)

- Specification
 - Write a specification for the circuit
 - i.e., the problem statement that describes the input-output requirement)
- Formulation
 - Derive the truth table or initial Boolean equations that define the required relationships between inputs and outputs
 - Convert problem statement to these form for optimization of circuit

Design procedures (3)

- Optimization
 - Apply two-level and/or **multiple-level** optimization, and
 - Draw a logic circuit diagram for the resulting circuit using AND, OR and NOT gates
 - Techniques: algebraic manipulation, K-map
- Technology mapping
 - Transform the logic circuit diagram to a new diagram using the available implementation technology
- Verification
 - Verify the correctness of the final design

Outline

- Combinational circuit design procedures
- **BCD-to-excess-3 code converter**
- BCD-to-seven-segment decoder
- Hierarchical design
- Technology mapping and verification

BCD-to-excess-3 code converter (1)

- Specification

- BCD: binary-coded decimals

- Excess-3-code

- Each decimal has its excess-3-code
- Binary combination of the decimal **plus 3**
- Example: Excess-3-code of 5 is 1000

- Requirement

- A converter which converts the BCD of a digit to its excess-3-code
- Input and output digits represented in binary format
 - Input: ABCD
 - Output: WXYZ
- I.e., Input of the converter: A, B, C and D;
- Output of the converter: W, X, Y and Z

BCD-to-excess-3 code converter (2)

- Formulation

- Derive the truth table for the converter
- 4 variables as BCD **input**, $2^4 = 16$ possible input combinations
 - However, combinations from 1010 to 1111 are invalid BCD code; assume they never happen and are don't care conditions
- Add 3, i.e., 0011 in binary, to the BCD input to obtain the excess-3-code, as **output**

BCD-to-excess-3 code converter (3)

TABLE 3-1
Truth Table for Code Converter Example


Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

BCD-to-excess-3 code converter (4)

- Optimization

- 4 input variables, hence use 4-variable K-map
- One output requires one K-map
 - i.e., 4 K-maps are required
 - Reason: one output is represented by one Boolean function
- Place 1s into the squares of K-map according to the 1s in the truth table
- Place Xs into the squares of K-map which represent don't care minterms
- Optimize the four Boolean functions
 - Place rectangles to include all 1s in the K-maps

BCD-to-excess-3 code converter (5)

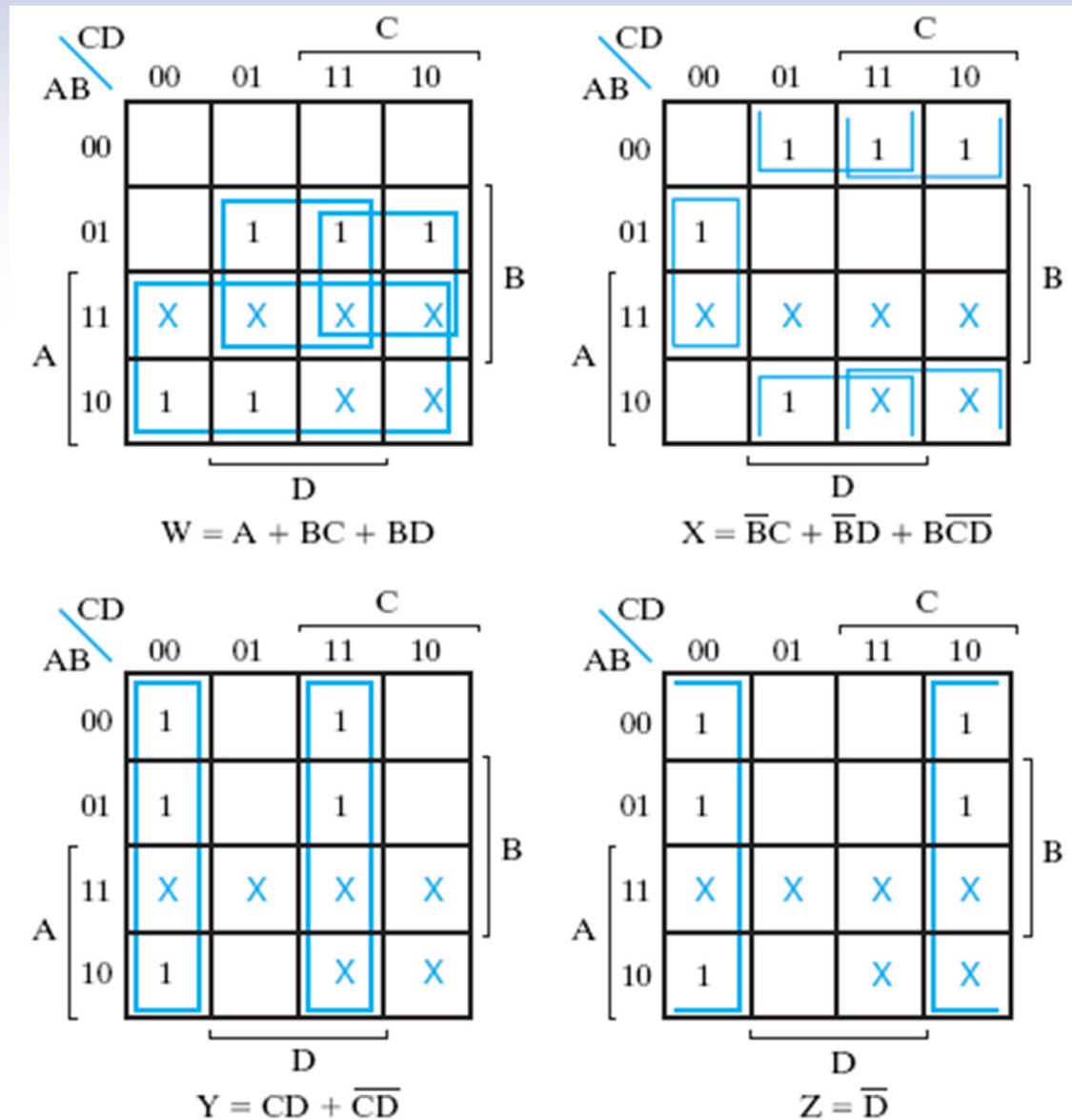

BCD-to-excess-3 code converter (6)

- Optimization

- Apply **multiple-level** optimization to reduce the gate input cost
 - Sharing of same terms among outputs

Boolean functions from K-map result


$$W = A + BC + BD$$

$$X = \overline{B}C + \overline{B}D + B\overline{C}\overline{D}$$

$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

 Gate-input cost:
26 (incl. inverters)
23 (excl. inverters)



Sharing terms among four outputs

$$T_1 = C + D$$

$$W = A + BC + BD = A + BT_1$$

$$X = \overline{B}C + \overline{B}D + B\overline{C}\overline{D} = \overline{B}T_1 + B\overline{C}\overline{D}$$


$$Y = CD + \overline{C}\overline{D}$$

$$Z = \overline{D}$$

Gate-input cost:
22 (incl. inverters)
19 (excl. inverters)

BCD-to-excess-3 code converter (7)

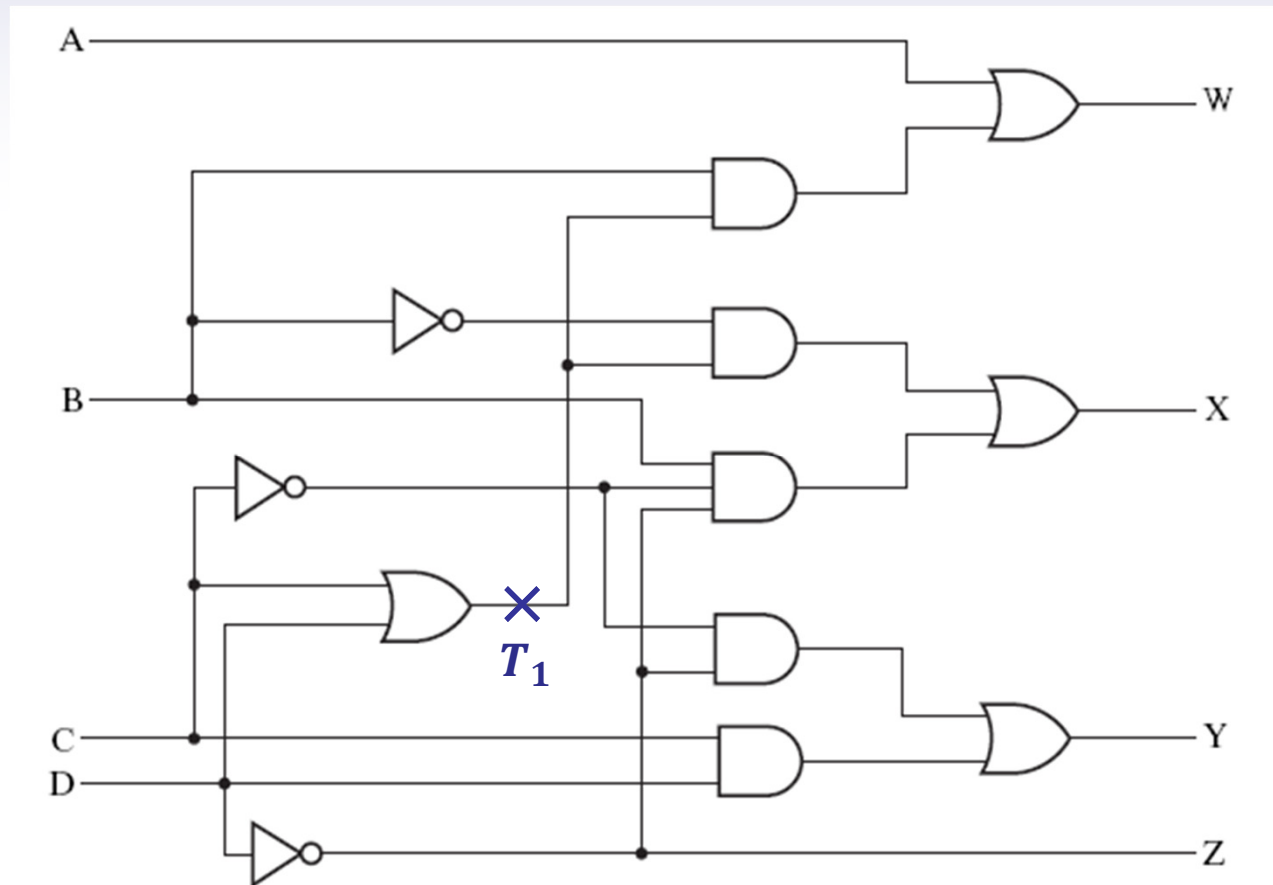Logic circuit diagram of BCD-to-excess-3 code converter



Outline

- Combinational circuit design procedures
- BCD-to-excess-3 code converter
- **BCD-to-seven-segment decoder**
- Hierarchical design
- Technology mapping and verification

BCD-to-seven-segment decoder (1)

- Specification


- BCD: binary-coded decimals

- Seven-segment

- A display consists of seven LED segments
- Each LED segment can be turned on by a digital signal
- E.g., alarm clock, calculator

- Requirement

 - A combinational circuit which accepts BCD digits as input, and generates appropriate outputs for the segment display to show the decimal digit
- Inputs: A, B, C and D; outputs: a, b, c, d, e, f and g



(a) Segment designation



(b) Numeric designation for display

BCD-to-seven-segment decoder (2)

- Formulation

- Derive the truth table for the decoder
- 4 variables as BCD **input**, $2^4 = 16$ possible input combinations
 - Combinations 1010 through 1111 have no meaning in BCD; can assume them to be don't care minterms
 - Now we use a safer choice – turn off all segments for these unused combinations
- **Output** 1 or 0 at the segment output (*a* to *g*) based on BCD input, so that decimal digit is displayed correctly
 - Assumption: output logic 1 means turning on the segment, logic 0 means turning off the segment

BCD-to-seven-segment decoder (3)

Truth Table for BCD-to-Seven-Segment Decoder

BCD Input				Seven-Segment Decoder						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
All other inputs				0	0	0	0	0	0	0

Turn off all LEDs
if BCD input is
invalid ←

BCD-to-seven-segment decoder (4)

- Optimization

- 4 input variables, hence use 4-variable K-maps
- 7 K-maps are required, one for each output
- Use normal K-map manipulation method to simplify the output functions

$$a = \overline{A}C + \overline{A}BD + \overline{B} \overline{C} \overline{D} + A\overline{B} \overline{C}$$

$$b = \overline{A} \overline{B} + \overline{A} \overline{C} \overline{D} + \overline{A}CD + A\overline{B} \overline{C}$$

$$c = \overline{A}B + \overline{A}D + \overline{B} \overline{C} \overline{D} + A\overline{B} \overline{C}$$

$$d = \overline{A}C\overline{D} + \overline{A} \overline{B}C + \overline{B} \overline{C} \overline{D} + A\overline{B} \overline{C} + \overline{A}B\overline{C}D$$

$$e = \overline{A}C\overline{D} + \overline{B} \overline{C} \overline{D}$$

$$f = \overline{A}B\overline{C} + \overline{A} \overline{C} \overline{D} + \overline{A}B\overline{D} + A\overline{B} \overline{C}$$

$$g = \overline{A}C\overline{D} + \overline{A} \overline{B}C + \overline{A}B\overline{C} + A\overline{B} \overline{C}$$

BCD-to-seven-segment decoder (5)

- Optimization

- Gates required: 27 AND gates and 7 OR gates
 - Number of product terms = number of AND gates required
 - Each output function requires an OR gate
- Possible to reduce the number of required gates
 - Sharing product terms
 - Reduction of 13 AND gates

Shared product terms	Occurrence	# gates reduced
$A \bar{B} \bar{C}$	6 (a, b, c, d, f, g)	5
$\bar{B} \bar{C} \bar{D}$	4 (a, c, d, e)	3
$\bar{A} C \bar{D}$	3 (d, e, g)	2
$\bar{A} \bar{C} \bar{D}$	2 (b, f)	1
$\bar{A} \bar{B} C$	2 (d, g)	1
$\bar{A} B \bar{C}$	2 (f, g)	1

Outline

- Combinational circuit design procedures
- BCD-to-excess-3 code converter
- BCD-to-seven-segment decoder
- **Hierarchical design**
- Technology mapping and verification

Hierarchical design

- Divide-and-conquer approach
- Use a *hierarchy* of symbols to represent the circuit
 - Entire circuit broken down into pieces called *blocks*
 - At lower level, blocks are implemented using primitive logic gates
 - Blocks are interconnected, to form a circuit which satisfies the problem specification
- Suitable for problem that
 - Has large number of inputs;
 - Too many inputs → using K-map approach is difficult
 - Can be broken down into smaller pieces

4-bit equality comparator (1)

- Specification

- Equality comparator compares two *binary vectors* (i.e., binary number)
- Returns 1 if the two input vectors are equal, 0 otherwise
- **Inputs:** A(3:0) and B(3:0)
 - i.e., two 4-bit numbers
 - $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$
- **Output:** E (one bit), the comparison result

- Example

- If A = 1000 and B = 1000, then E = 1
- If A = 1001 and B = 1000, then E = 0

4-bit equality comparator (2)

- Formulation

- Possible to break down the problem...

- If each bit position of A and B are equal in ALL four positions, then $E = 1$
- Compare a bit from A with the corresponding bit from B
- Repeat the comparison for every bit positions
- Combine the result and output E

- Not necessary to construct truth tables


- Otherwise, we have 8 inputs
 - ($2^8 = 256$ input combinations!)

4-bit equality comparator (3)

- MX: one-bit comparison circuit

- Input: A_i, B_i
- Output: N_i

- ME: combines N_i and gives E

 

(a)

4-bit equality comparator (4)

- Optimization, two approaches
 - Approach 1
 - In each MX circuit, $N_i = 1$ if A_i and B_i are different
 - In ME circuit, output $E = 0$ if one of the N_i is 1
 - Approach 2
 - In each MX circuit, $N_i = 1$ if A_i and B_i are the same
 - In ME circuit, output $E = 1$ if all N_i is 1

Approach 1

$$N_i = \overline{A_i} B_i + A_i \overline{B_i}$$

$$E = \overline{N_0 + N_1 + N_2 + N_3}$$


Approach 2

$$N_i = A_i B_i + \overline{A_i} \overline{B_i}$$

$$E = N_0 N_1 N_2 N_3$$

4-bit equality comparator (5)


Logic circuit diagram using approach 1

 

MX circuit for one bit comparison

ME circuit for output E

Structure of hierarchy

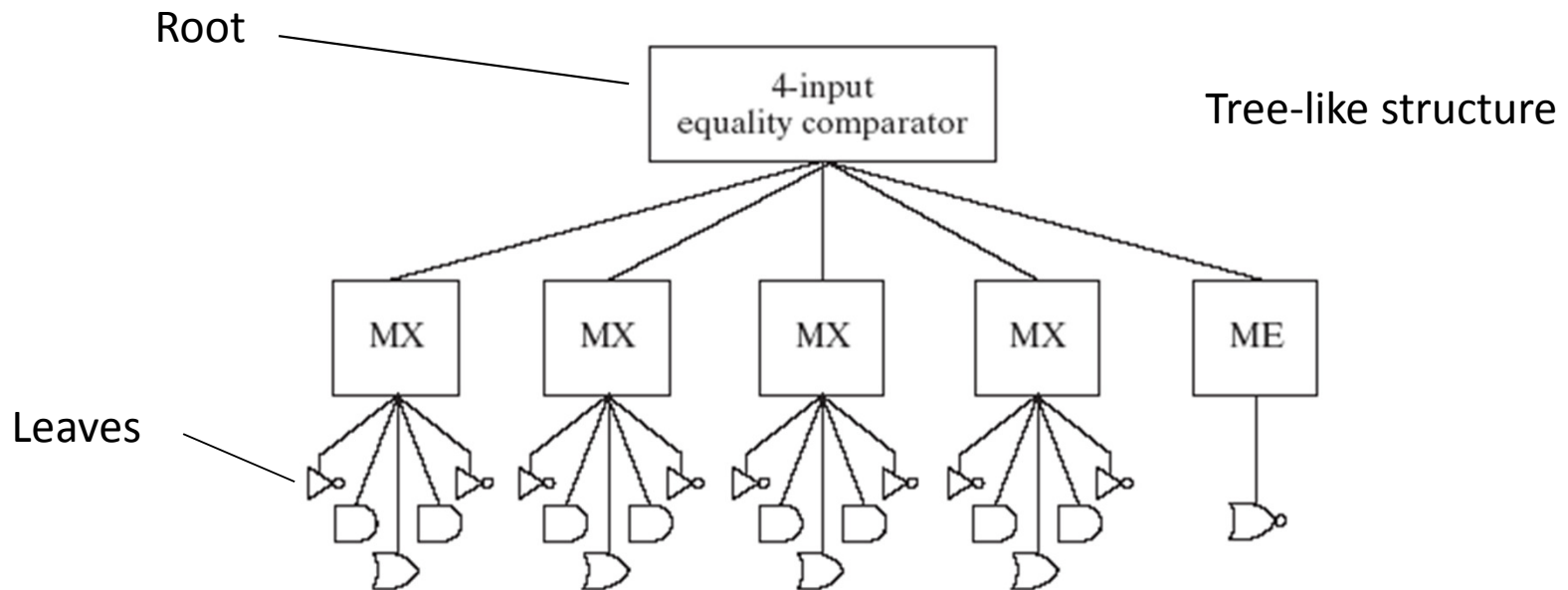

Hierarchical design

- Simpler circuit diagram can be drawn
 - An MX circuit block represents a circuit that uses 5 gates
 - Reduces the number of symbols in the diagram
- Allows reuse of blocks
 - In the previous example, the MX circuit is reused four times

Outline


- Combinational circuit design procedures
- BCD-to-excess-3 code converter
- BCD-to-seven-segment decoder
- Hierarchical design
- Technology mapping and verification

Technology mapping (1)


- Mapping of a logic circuit diagram to a description that uses the available implementation technology
 - NAND or NOR gates are mostly available
- Map AND, OR and NOT gates to either NAND, or NOR gate description
 - Fixed number of input (n) in NAND or NOR gates
 - If $n = 1$, the NAND gate is represented by an inverter (NOT gate)

Technology mapping (2)

 - With an optimized logic diagram with AND, OR gates and inverters, convert the logic functions to NAND logic (or NOR logic)
- Procedures
 - (1) Replace AND and OR gate with NAND (NOR) gate and inverter




(a) Mapping to NAND gates

 

 
(b) Mapping to NOR gates

Technology mapping (3)

- Procedures
 - (2) Push inverters through a dot
 - (3) Cancel inverter pairs
 - So that between two NAND gates there is at most one inverter



(c) Pushing an inverter through a "dot"

 

(d) Cancelling inverter pairs


Technology mapping (4)

- Example: implement F with NAND gates

$$F = AB + \overline{A}BC + \overline{A}\overline{B}\overline{D} + E$$


- Step 1: Replace AND and OR gates with NAND gates and inverters (figure b)

 (a) Logic diagram of F using AND gates, OR gates and inverters



(a)

(b) Logic diagram of F after step 1

 

(b)

Verification

- Verification of circuit function
 - Determine whether a given circuit implements its specified function by logic analysis
 - Important in preventing incorrect circuit design from being manufactured and used
- Two approaches
 - Manual logic analysis
 - Computer simulation-based logic analysis

Manual logic analysis


- Based on a logic circuit diagram in NAND gate implementation
 - (1) Find the Boolean equations for each output of the circuit
 - (2) Find the truth table for the circuit
 - (3) Verify the derived truth table, compare with the original truth table specification

BCD-to-excess-3 code converter verification (1)

(a) Original truth table specification; (b) final NAND-mapped circuit implementation

Input BCD				Output Excess-3			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

(a)

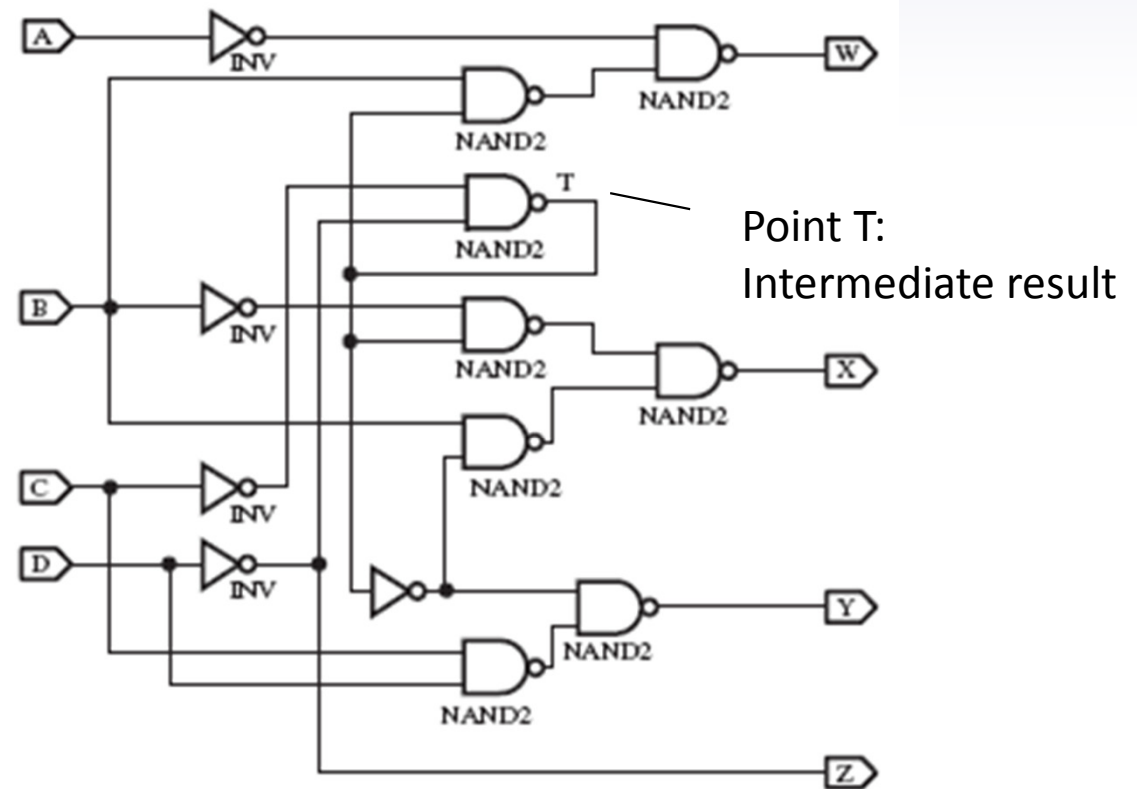

(b)

BCD-to-excess-3 code converter verification (2)

- Determine equations for outputs W, X, Y and Z
 - Intermediate point T is used
 - Ease the verification process
- Substitute expression for T in equations for W, X and Y

NAND operation:

$$\overline{XY} = \overline{X} + \overline{Y}$$

$$T = \overline{\overline{C} \overline{D}} = C + D$$

$$W = \overline{\overline{A}(\overline{TB})} = A + BT$$

$$X = \overline{(\overline{BT})(\overline{BT})} = \overline{BT} + B\overline{T}$$

$$Y = CD + \overline{T}$$

$$Z = \overline{D}$$

$$W = A + B(C + D) = A + BC + BD$$

$$X = \overline{B}(C + D) + B(\overline{C} \overline{D})$$

$$= \overline{B}C + \overline{B}D + B\overline{C} \overline{D}$$

$$Y = CD + \overline{C} \overline{D}$$

$$Z = \overline{D}$$

BCD-to-excess-3 code converter verification (3)

- Derive the truth table, and verify with the original truth table
 - Determine output W, X, Y and Z under each possible input combinations
 - Place 1s in the truth table which map with the product term in output equations W, X, Y and Z

Partially filled truth table, only the following product terms are placed:

$$A, BC, BD, \overline{BC}, CD, \overline{D}$$


Input BCD				Output Excess-3			
A	B	C	D	W	X	Y	Z
0	0	0	0				1
0	0	0	1				
0	0	1	0		1		1
0	0	1	1		1	1	
0	1	0	0				1
0	1	0	1	1			
0	1	1	0	1			1
0	1	1	1	1		1	
1	0	0	0	1			1
1	0	0	1	1			

Simulation-based logic analysis (1)

- Output of a circuit generated by computer through simulation
 - Suitable for circuit with large number of input variables
- Verification process
 - **Input circuit** implementation to simulator
 - **Enter input combinations** in the form of a waveform (INPUT section)
 - **Simulator gives** corresponding **output** waveform (OUTPUT section)
 - **Verify** whether output match with original truth table

Simulation-based logic analysis (2)

 $(A,B,C,D) = (0,0,0,0)$ $(A,B,C,D) = (0,0,0,1)$ $(A,B,C,D) = (0,0,1,0)$



$(W,X,Y,Z) = (0,0,1,1)$ $(W,X,Y,Z) = (0,1,0,0)$ $(W,X,Y,Z) = (0,1,0,1)$

Summary and acknowledgment

- A five-step design procedure for combinational circuit was discussed and illustrated with examples
- Concept of design hierarchy was introduced
- Optimization step applies two-level and multiple-level optimization
- Technology mapping converts the circuit into one which uses NAND or NOR gates only
- Verification through logic analysis assures the final circuit satisfies the initial specification
- Reference
 - Logic and Computer Design Fundamental (5/e)